

July 28, 2019

### Series and parallel connection of capacitors

**Data:**

#### Series

C (Capacitors in series)	V (volts) measured	Q (coulomb) = CV
$C_1 = 100 \mu\text{F}$	5.17 V	$(5.17 * 10^{-4}) \text{ C}$
$C_2 = 330 \mu\text{F}$	1.68 V	$(5.544 * 10^{-4}) \text{ C}$
	$V_{\text{batt}} = 9$	$Q_{\text{av}} = (5.357 * 10^{-4}) \text{ C}$
$C_{\text{eq}} = Q_{\text{av}}/V_{\text{batt}}$	$C_{\text{eq}} (\text{measured}) = (5.952 * 10^{-5}) \text{ F}$	
$1/C_{\text{eq}} = 1/C_1 + 1/C_2$	$C_{\text{eq}} (\text{predicted}) = (7.67442 * 10^{-5}) \text{ F}$	

#### **Calculations:**

Converting  $\mu\text{F}$  to F:  $C_1 = (100 * 10^{-6}) = (1 * 10^{-4}) \text{ F}$ ;  $C_2 = (330 * 10^{-6}) = (3.3 * 10^{-4}) \text{ F}$

Calculating Q:  $Q_1 = (1 * 10^{-4}) * (5.17) = (5.17 * 10^{-4}) \text{ C}$

$Q_2 = (3.3 * 10^{-4}) * (1.68) = (5.544 * 10^{-4}) \text{ C}$

Calculating  $Q_{\text{av}} = (5.17 * 10^{-4}) + (5.544 * 10^{-4}) = (.0010714)/2 = (5.357 * 10^{-4}) \text{ C}$

Calculating  $C_{\text{eq}} (\text{measured}) = (5.357 * 10^{-4})/(9) = (5.952 * 10^{-5}) \text{ F}$

Calculating  $C_{\text{eq}} (\text{predicted}) = 1/C_{\text{eq}} = (1/(1 * 10^{-4})) + (1/(3.3 * 10^{-4})) = 13030.30303 \text{ F}$

$C_{\text{eq}} (\text{predicted}) = (13030.30303)^{-1} = (7.67442 * 10^{-5}) \text{ F}$

$V_{\text{tot}} = V_1 + V_2: (5.17) + (1.68) = 6.85 \text{ V}$

#### Parallel

C (Capacitors in parallel)	V (volts) measured	Q (coulomb) = CV
----------------------------	--------------------	------------------

$C_1 = 100 \mu\text{F}$	7.03	$(7.03 * 10^{-4}) \text{ C}$
$C_2 = 330 \mu\text{F}$	7.03	$(2.32 * 10^{-3}) \text{ C}$
$C_{\text{eq}} (\text{measured}) = Q_{\text{total}}/V_{\text{batt}}$	$V_{\text{batt}} = 9$	$Q_{\text{tot}} = .0030229 \text{ C}$
$C_{\text{eq}} = Q_{\text{tot}}/V_{\text{batt}}$	$C_{\text{eq}} (\text{measured}) = (3.35878 * 10^{-4}) \text{ F}$	
$C_{\text{eq}} = C_1 + C_2$	$C_{\text{eq}} (\text{predicted}) = (4.3 * 10^{-4}) \text{ F}$	

### Calculations:

Converting  $\mu\text{F}$  to F:  $C_1 = (100 * 10^{-6}) = (1 * 10^{-4}) \text{ F}$ ;  $C_2 = (330 * 10^{-6}) = (3.3 * 10^{-4}) \text{ F}$

Calculating Q:  $Q_1 = (1 * 10^{-4}) * (7.03) = (7.03 * 10^{-4}) \text{ C}$

$$Q_2 = (3.3 * 10^{-4}) * (7.03) = (.0023199) \text{ C or } (2.32 * 10^{-3}) \text{ C}$$

Calculating  $Q_{\text{tot}} = Q_1 + Q_2$ :  $(7.03 * 10^{-4}) + (2.32 * 10^{-3}) = .0030229$

Calculating  $C_{\text{eq}} = Q_{\text{tot}}/V_{\text{batt}}$ :  $C_{\text{eq}} (\text{measured}) = (.0030229)/(9) = (3.35878 * 10^{-4}) \text{ F}$

Calculating  $C_{\text{eq}} = C_1 + C_2$ :  $C_{\text{eq}} (\text{predicted}) = (1 * 10^{-4}) + (3.3 * 10^{-4}) = (4.3 * 10^{-4}) \text{ F}$

### Analysis:

So, with the circuit wired in series we can see that the voltages differ across the capacitors. With the total voltage equaling to 6.85 V. The Q (Charges in Coulombs) also come out to about the

same, which is expected for a circuit wired in series. Also, for a circuit in series, the equivalent capacitance was the inverse of one over each specific capacitance. We predicted (calculated) that this would be  $(7.67442 * 10^{-5})$  F. We measured it to be  $(5.952 * 10^{-5})$  F. They are about .00001 off. This could be due to the measured voltage not being exactly 9V so when using the equation  $C_{eq} = Q_{av}/V_{batt}$  it could throw our calculation off. On the other hand if we used the  $V_{tot}$  we measured which was about 6.85 V, we can calculate, again, the  $C_{eq}$ . Which would look like this ( $C_{eq} = (5.357 * 10^{-4})/(6.85) = 7.82044 * 10^{-5}$ ). Which is more in line with our prediction/calculation.

With the circuit wired in parallel we can see that the voltages are the same across the capacitors. The total voltage we measured was 7.03 V. However, this time the Q (Charges in Coulombs) were different this time, which is expected for a circuit wired in parallel. Also, for a circuit in parallel, the equivalent capacitance was simply the specific capacitance of each capacitor added together. We predicted (calculated) that this would be  $(3.35878 * 10^{-4})$  F. We measured it to be  $(4.3 * 10^{-4})$  F. They are about .0001 off. This again, could be due to the measured voltage not being exactly 9V so when using the equation  $C_{eq} = Q_{tot}/V_{batt}$  it could throw our calculation off. On the other hand if used the Voltage that we measured (Which is the same regardless of where you measure it in a parallel series) which was 7.03 V, we can calculate, again, the  $C_{eq}$ . Which would look like this ( $C_{eq} = (.0030229)/(7.03) = 4.3 * 10^{-4}$ ). Which is exactly what our prediction/calculation was.